

Electrifying The World!

(T)


What is Electricity?

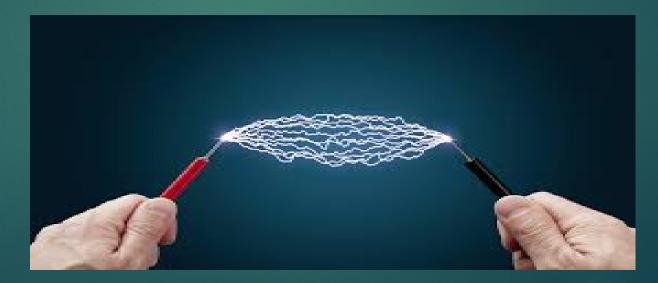

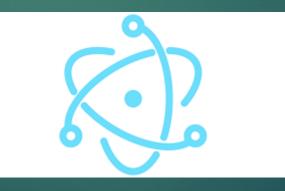What type of charge does an electron have ?



What is a circuit?

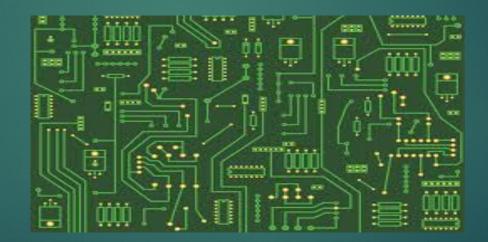

Let's Act It out!

Casting

Teacher: Battery Students: the path Objects: electrons

Creation Station!

- ► What are we creating ? Students will create a circuit
- ► How long will we have ? 10 minutes (Stay on task)
- ► Instructions
- Step1) each student team take a battery, a light bulb, light bulb holder and a piece of wire.
- Step2) Using wire strippers or sandpaper, carefully remove about 1/4-3/8 in (approximately 6-10 mm) of insulation from the ends of the wire.
- Step3) Try to connect the battery, light bulb, light bulb holder and wire so the bulb lights up. Use tape if necessary. Hint: Which way do electrons flow?

Would This Work?



Would This Work?



Would This Work?







What are some real life examples of a circuit?

Lets evaluate !

Complete the evaluation worksheet on your own.
Turn in your worksheet once you are done